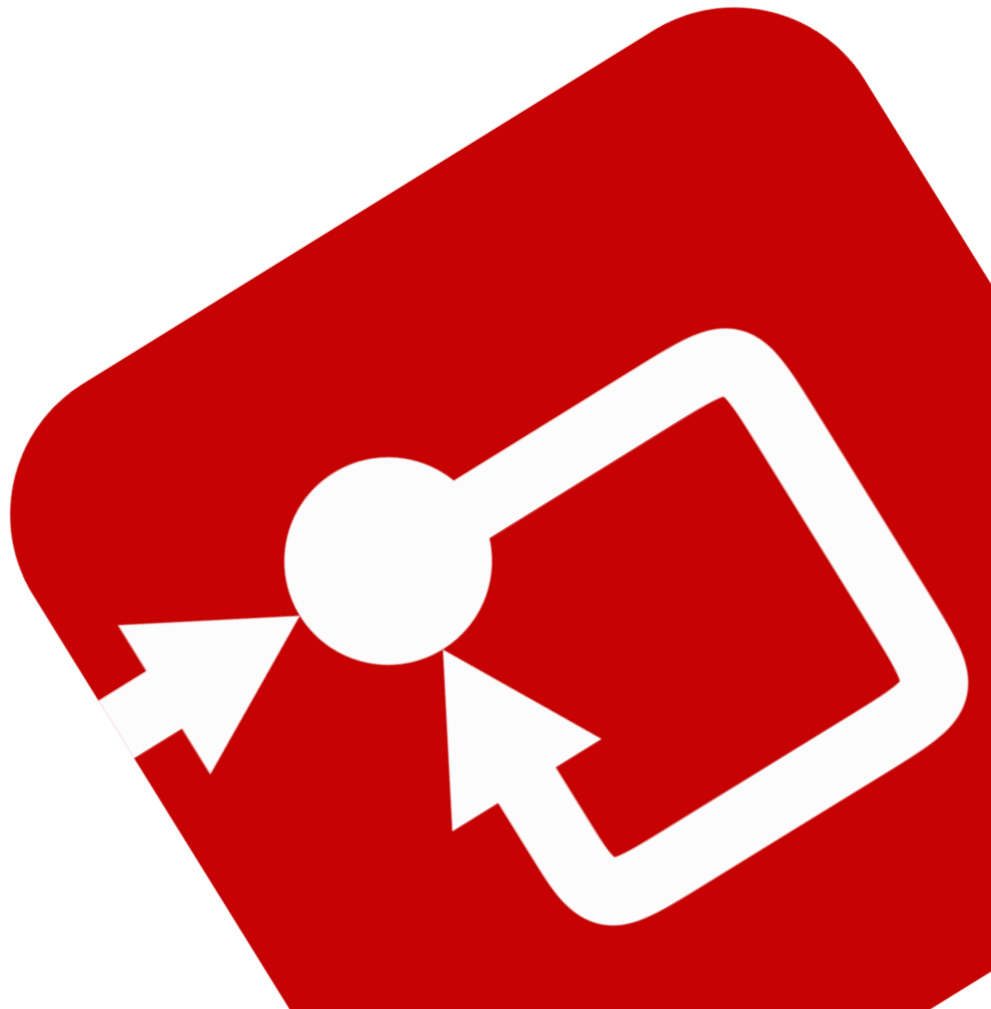


smart
ctrl

control design for power electronics

Single Control Loop Design

Tutorial –December 2018–



How to Contact:



info@powersmartcontrol.com



www.powersmartcontrol.com

SmartCtrl Copyright © 2015-2018 Power Smart Control S.L.

All Rights Reserved.

No part of this tutorial may be reproduced or modified in any form or by any means without the written permission of Power Smart Control S.L.

Notice

Power Smart Control tutorials or other design advice, services or information, including, but not limited to, reference designs, are intended to assist designers who are developing applications that use SmartCtrl; by downloading, accessing or using any particular Power Smart Control resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this notice.

Power Smart Control reserves the right to make corrections, enhancements, improvements and other changes to its resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications with all applicable regulations, laws and other applicable requirements.

Disclaimer

Power Smart Control S.L. (PSC) makes no representation or warranty with respect to the adequacy or accuracy of this documentation or the software which it describes. In no event will PSC or its direct or indirect suppliers be liable for any damages whatsoever including, but not limited to, direct, indirect, incidental, or consequential damages of any character including, without limitation, loss of business profits, data, business information, or any and all other commercial damages or losses, or for any damages in excess of the list price for the licence to the software and documentation.

The software SmartCtrl© used in this tutorial is furnished under a license agreement. The software may be used only under the terms of the license agreement.



General index

1. Introduction.....	3
2. Buck converter design.....	4
3. Design exportation to Psim.....	12
4. Design validation.....	13

Figure index

Figure 1: Desired system.....	3
Figure 2: SmartCtrl initial window.....	4
Figure 3: Alternative access to design a Voltage controlled DC-DC converter.....	4
Figure 4: Defining the converter analog topology.....	5
Figure 5: Plant parameters.....	5
Figure 6: choosing the sensor.....	6
Figure 7: Defining the sensor.....	6
Figure 8: Choosing the compensator.....	7
Figure 9: Solution map quick comparison between type 2 and 3 controllers.....	7
Figure 10: Choosing Type 3 compensator.....	8
Figure 11: configuring Type 3 compensator.....	8
Figure 12: Access to the solution map.....	9
Figure 13: Defining a point in the solution map.....	9
Figure 14: converter definition window.....	10
Figure 15: SmartCtrl results window.....	10
Figure 16: Report buttons.....	11
Figure 17: input and output data reports.....	11
Figure 18: Exportation to Psim button.....	12
Figure 19: exportation to Psim settings.....	12
Figure 20: Psim exported system.....	13
Figure 21: clock configuration in Psim.....	13
Figure 22: result of Psim simulation.....	14
Figure 23: input voltage step in Psim.....	14
Figure 24: New Psim simulation where dynamic response can be seen.....	15

1. Introduction

This tutorial is intended to guide you, step by step, to design a DC/DC converter with a single control loop. The selected converter for this example is the buck converter included in Figure 1.

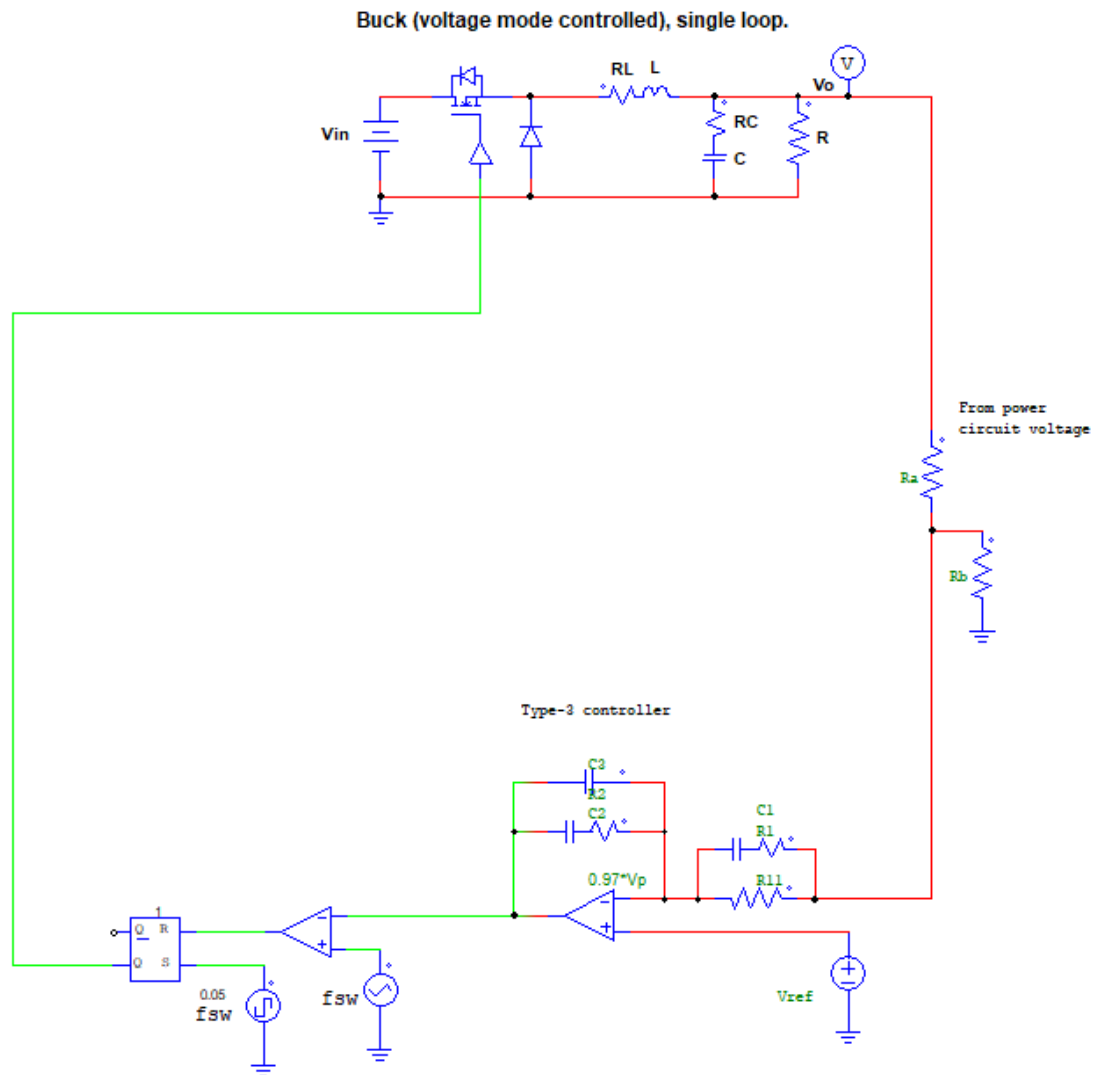


Figure 1: Desired system

2. Buck converter design

1. Open your SmartCtrl Software.
2. To begin the design of a single control loop DC/DC converter click on *DC-DC converter – single loop Voltage Mode Control or ACMC*. See Figure 2.

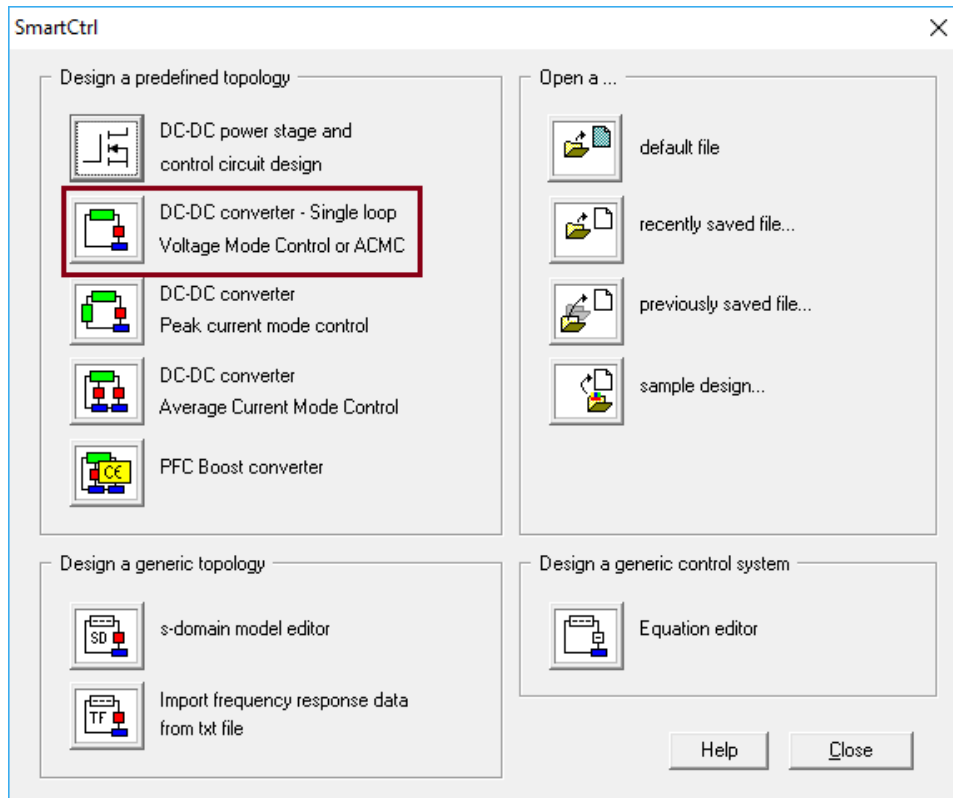



Figure 2: SmartCtrl initial window

It can also be accessed with:

- a) Button 
- b) Select the corresponding option within the Design menu. See Figure 3.

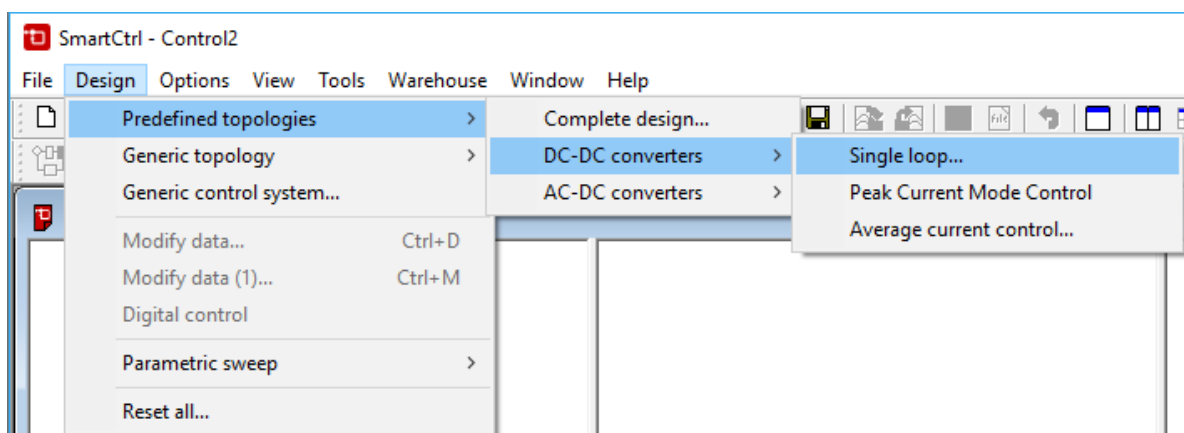


Figure 3: Alternative access to design a Voltage controlled DC-DC converter

3. Select a buck converter and parametrize it as follows. See Figure 4 and Figure 5.

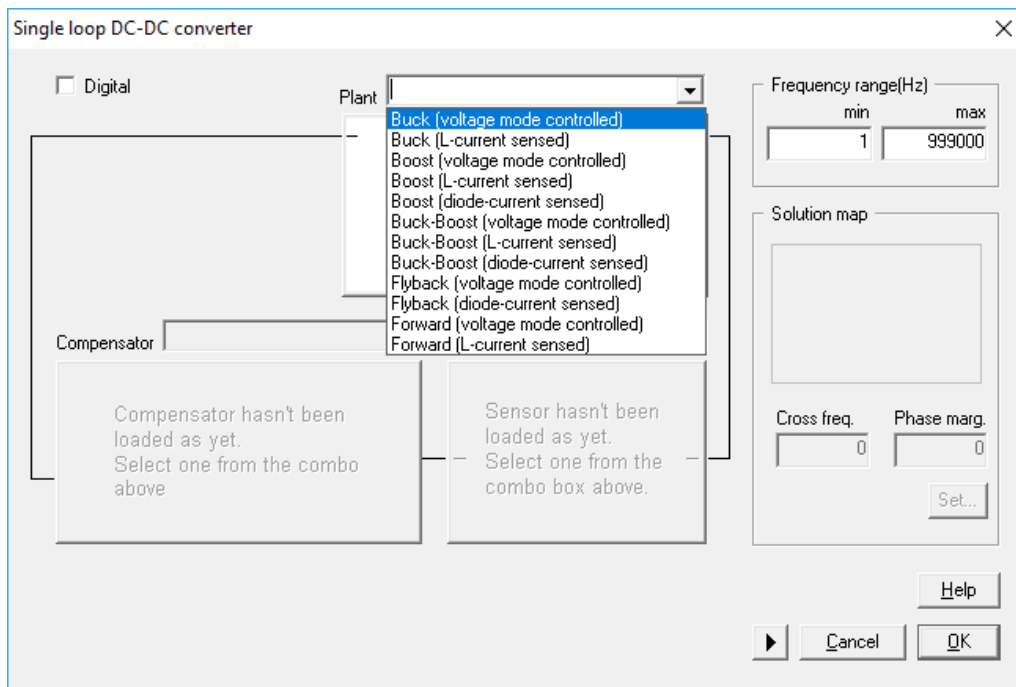


Figure 4: Defining the converter analog topology

As the design is controlled in an analog way, the checkbox “Digital” should be left unchecked. In case the design were digital controlled, it should be checked at this stage or further changes will be lost.

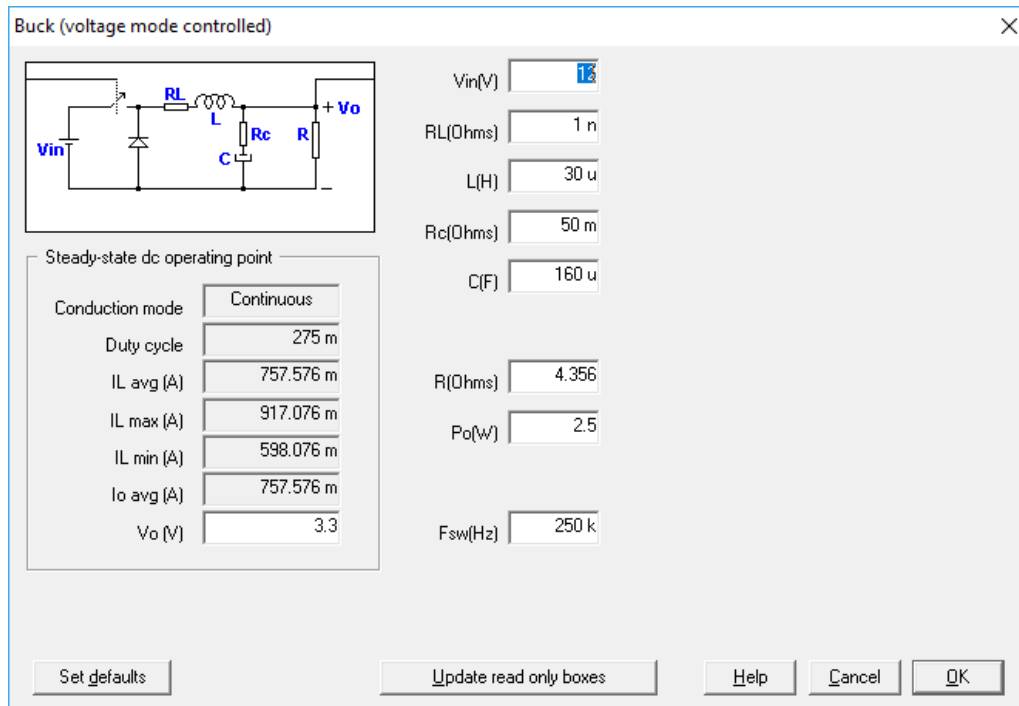


Figure 5: Plant parameters

4. Configure the sensor. See Figure 6 and Figure 7.

Once the plant has been selected, depending on which magnitude is going to be controlled, the program will display the appropriate type of sensors.

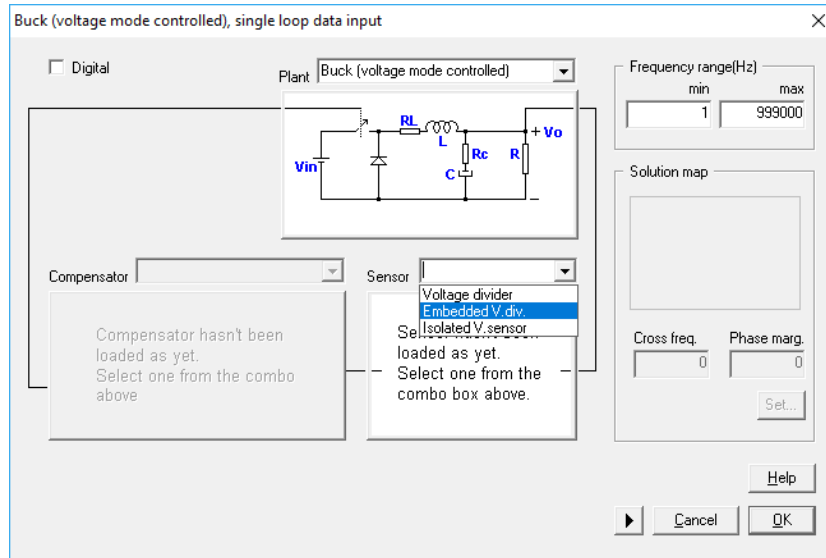


Figure 6: choosing the sensor

In the case of the voltage divider, the user should introduce the reference voltage and the program will automatically calculate the sensor gain. The sensor input data window is the following:

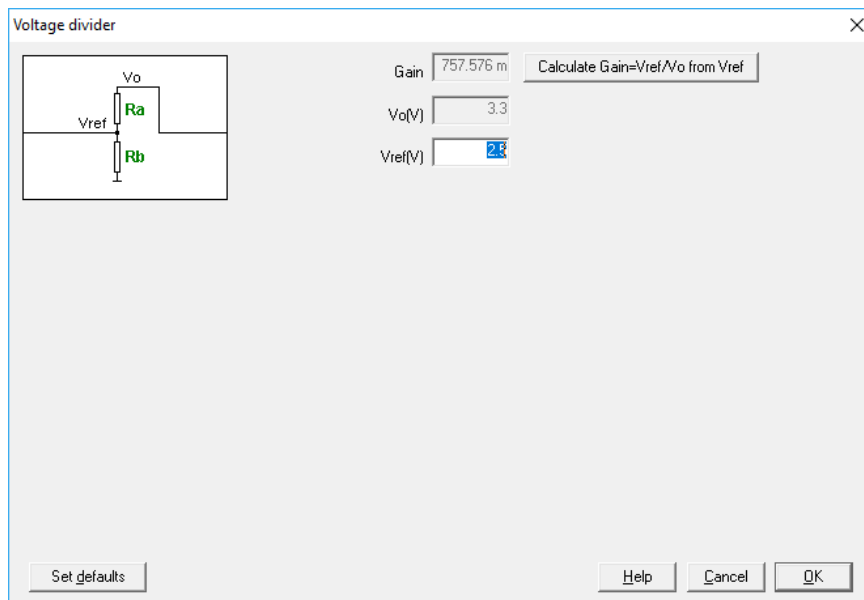


Figure 7: Defining the sensor

Click OK to continue.

Please, note that all the design process will be carried out using this gain, and the resistor values to implement the voltage divider will be provided by the program together with the regulator components.

5. Select and configure the compensator. See Figure 8.

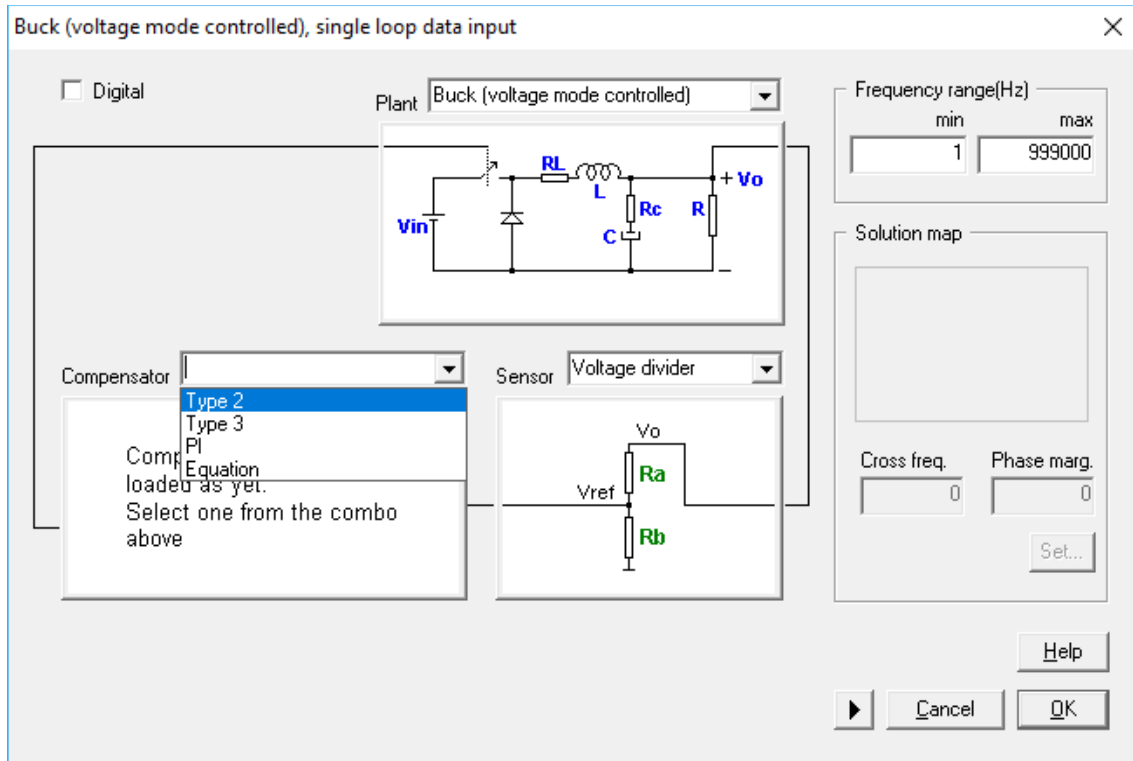


Figure 8: Choosing the compensator

As the design is analog controlled, only analog topologies are listed. To clarify this aspect a little bit a comparison between Type 2 and Type 3 compensators has been done. This comparison is made by means of the solution map. See Figure 9.

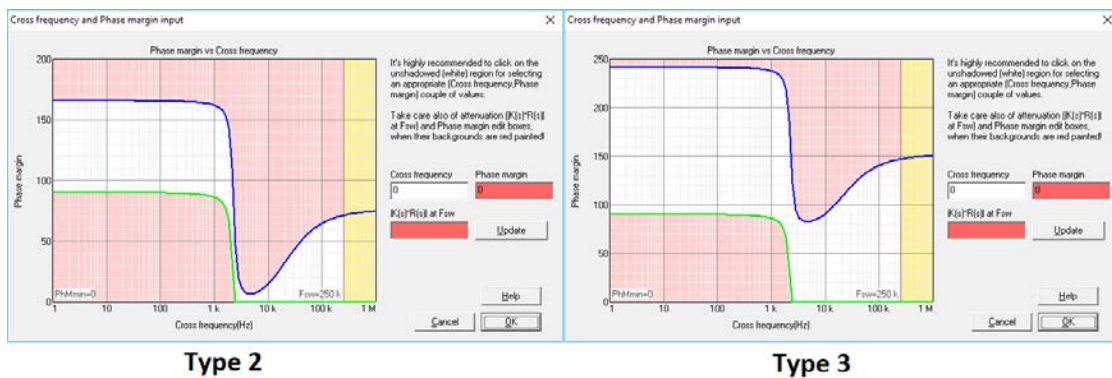


Figure 9: Solution map quick comparison between type 2 and 3 controllers

Due to the fact that the plant is a second order one, the best choice in order to obtain a proper phase margin and enough bandwidth is to use a Type 3 regulator as it provides the wider white area.

A remark should be done: the solution map window shows all the pairs *Phase Margin – cross Over Frequency*. All the ones contained in the white area will generate a perfectly stable controller. On the contrary, if chosen in the red area the controller will almost for sure be unstable.

In this tutorial, a Type 3 compensator has been chosen. So select the compensator type from the corresponding drop-down menu and parametrize it as done in Figure 10 and Figure 11.

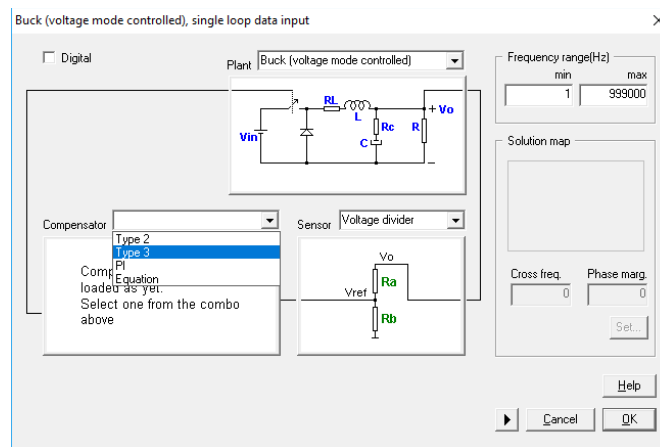


Figure 10: Choosing Type 3 compensator

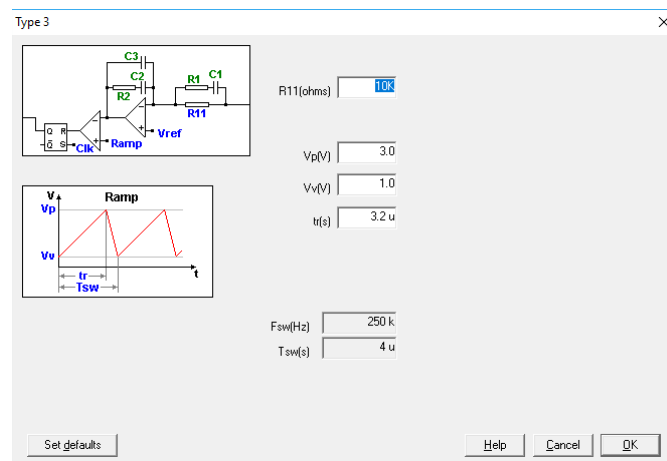


Figure 11: configuring Type 3 compensator

The fields V_p , V_v and t_r are referred to the modulator and all of them defined the gain of the modulator.

- Once the system has been defined, the crossover frequency and the phase margin of the open loop must be selected.

SmartCtrl provides a fast shortcut to select the crossover frequency and the phase margin called solutions map. This window has been partially introduced in the previous point.

Each point within the white area corresponds to a combination of cross freq. and phase margin that lead to a stable solution. In addition, when a point is selected, the attenuation given by the sensor and the regulator at the switching frequency is provided. Note that not enough attenuation at the switching frequency could provoke high frequency oscillations.

To carry out the selection just click on the “Set” button and SmartCtrl will display the solutions map. Then select a point within the white zone (left click) and click OK to continue. See Figure 12 and Figure 13.

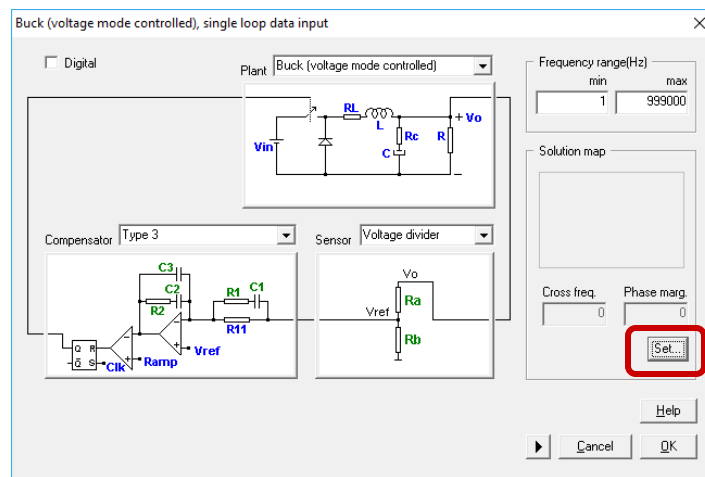


Figure 12: Access to the solution map

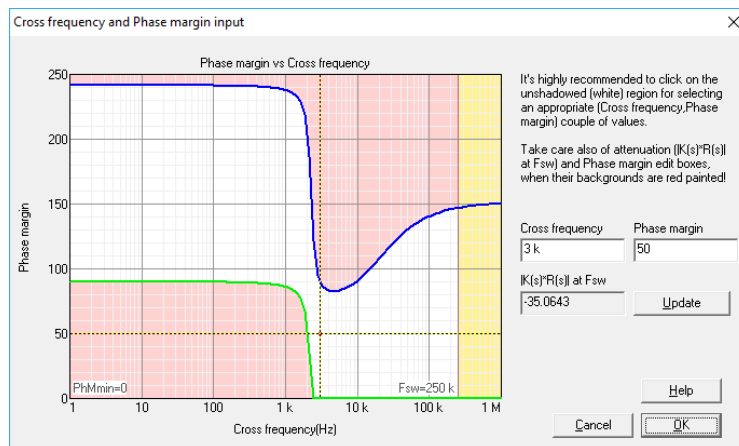


Figure 13: Defining a point in the solution map

All the points in the white area will be stable what will vary will be the dynamic response of the controller. As a rule of thumb, a good point for controlling is about:

- a) A phase margin of about 45 to 60 degrees
- b) A cross over frequency = Switching frequency/10

Please, notice this rule of thumb is not always achievable, but the nearest point in the white area will be good enough.

The solutions map will be shown on the right side of the input data window. See Figure 14.

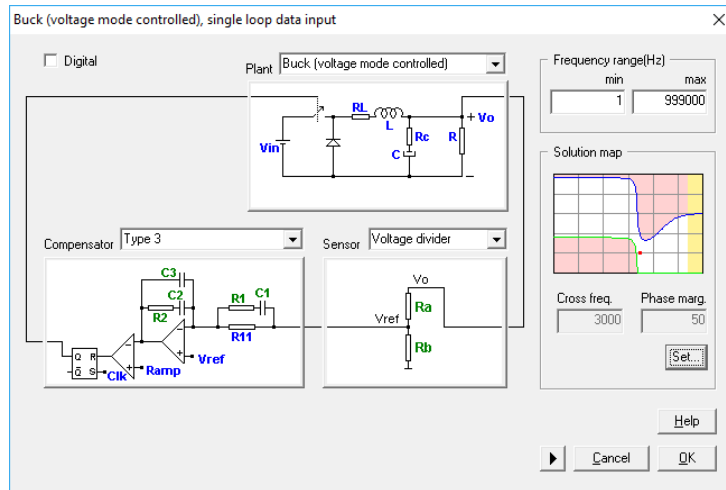


Figure 14: converter definition window

- 6. Click OK to confirm the design and the program will automatically show the performance of the system in terms of frequency response, Nyquist plot, transient response, etc. Additionally, optimization tools such as parametric sweep for sensibility analysis and control loop optimization algorithms, are provided. See the Figure 15.

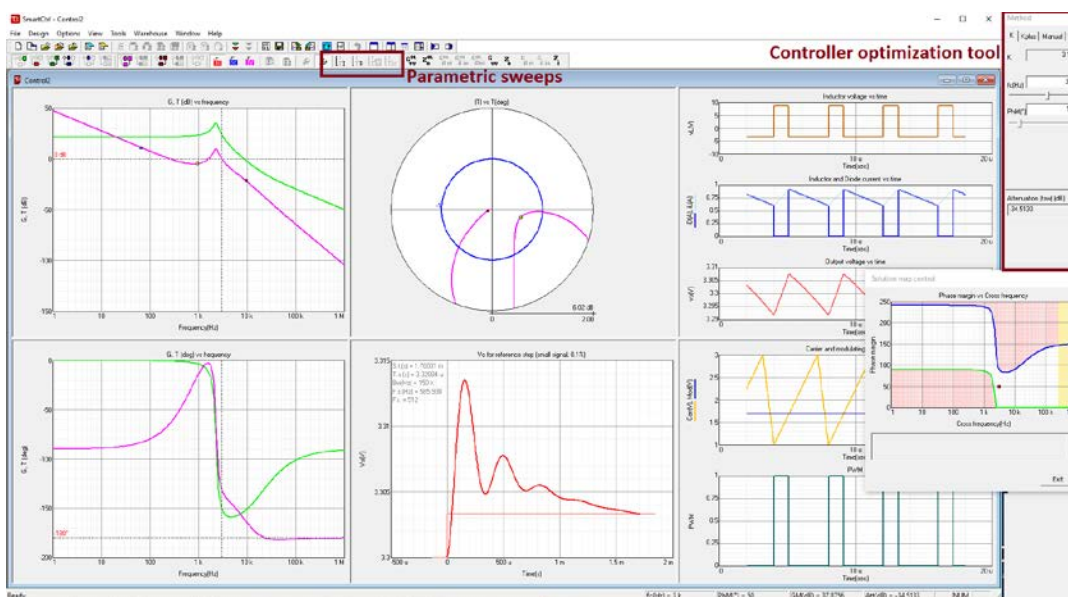


Figure 15: SmartCtrl results window

SmartCtrl also provides the components values needed to implement the compensator, the voltage divider resistors and the input parameters like the topology. To obtain those windows, click on the button of Figure 16 and Figure 17:



Figure 16: Report buttons

Output data	Input data
<p>RESULTS</p> <p>Compensator (Analog):</p> <hr/> <p>R1 (Ohms) = 1.13641 k R2 (Ohms) = 752.081</p> <p>C1 (F) = 14.9128 n C2 (F) = 220.82 n C3 (F) = 25.0943 n</p> <p>fz1 (Hz) = 958.333 fz2 (Hz) = 958.333 fp1 (Hz) = 9.39131 k fp2 (Hz) = 9.39131 k fi (Hz) = 64.7196</p> <p>b2 (s²) = 2.75808e-008 b1 (s) = 0.000332149 b0 = 1</p> <p>a3 (s³) = 7.06273e-013 a2 (s²) = 8.33505e-008 a1 (s) = 0.00245915 a0 = 0</p> <p>Sensor:</p> <hr/> <p>Ra (Ohms) = 1.056 k Rb (Ohms) = 3.3 k</p> <p>Pa (Watts) = 606.06 u Pb (Watts) = 1.89394 m</p> <p>Loop performance parameters:</p> <hr/> <p>PhF (Hz) = 23.0598 k GM (dB) = 37.8756 Atte(dB) = -34.5133</p>	<p>INPUT DATA</p> <p>Single loop</p> <hr/> <p>Frequency range (Hz) : (1, 999 k) Cross frequency (Hz) = 3 k Phase margin (°) = 50</p> <p>Plant</p> <hr/> <p>Buck (voltage mode controlled) R (Ohms) = 4.356 L (H) = 30 u RL(Ohms) = 1 n C (F) = 160 u RC(Ohms) = 50 m Vin (V) = 12 Vo (V) = 3.3 Fsw (Hz) = 250 k</p> <p>Steady-state dc operating point</p> <hr/> <p>Mode = Continuous Duty cycle= 0.275 Vcomp(V) = 1.6875 IL (A) = 757.576 m ILmax(A) = 917.076 m ILmin(A) = 598.076 m Io (A) = 757.576 m Vo (V) = 3.3</p> <p>Sensor</p> <hr/> <p>Voltage divider Vref/Vo = 0.757576</p> <p>Compensator</p> <hr/> <p>Type 3 Gmod = 0.4 R11(Ohms) = 10000 Vp(V) = 3 Vv(V) = 1 tr(sec) = 3.2e-006 Vref(V) = 2.5</p> <p>Steady-state dc operating point</p> <hr/> <p>IC_C3(V) = 812.501m IC_C2(V) = 812.501m IC_C1(V) = 0</p>

Figure 17: input and output data reports

3. Design exportation to Psim

To export to Psim click on this button. Figure 18.

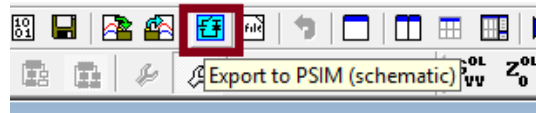


Figure 18: Exportation to Psim button

And configure the exportation. See Figure 19.

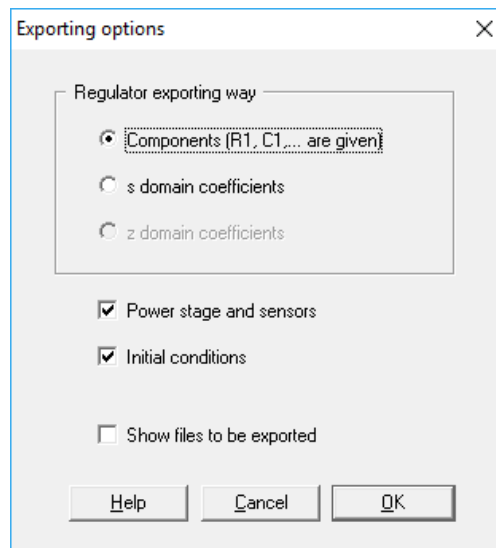


Figure 19: exportation to Psim settings

Click OK and Psim will be automatically opened and the simulation launched.

4. Design validation

In Psim, the following system has been automatically created and configured by SmartCtrl. See Figure 20.

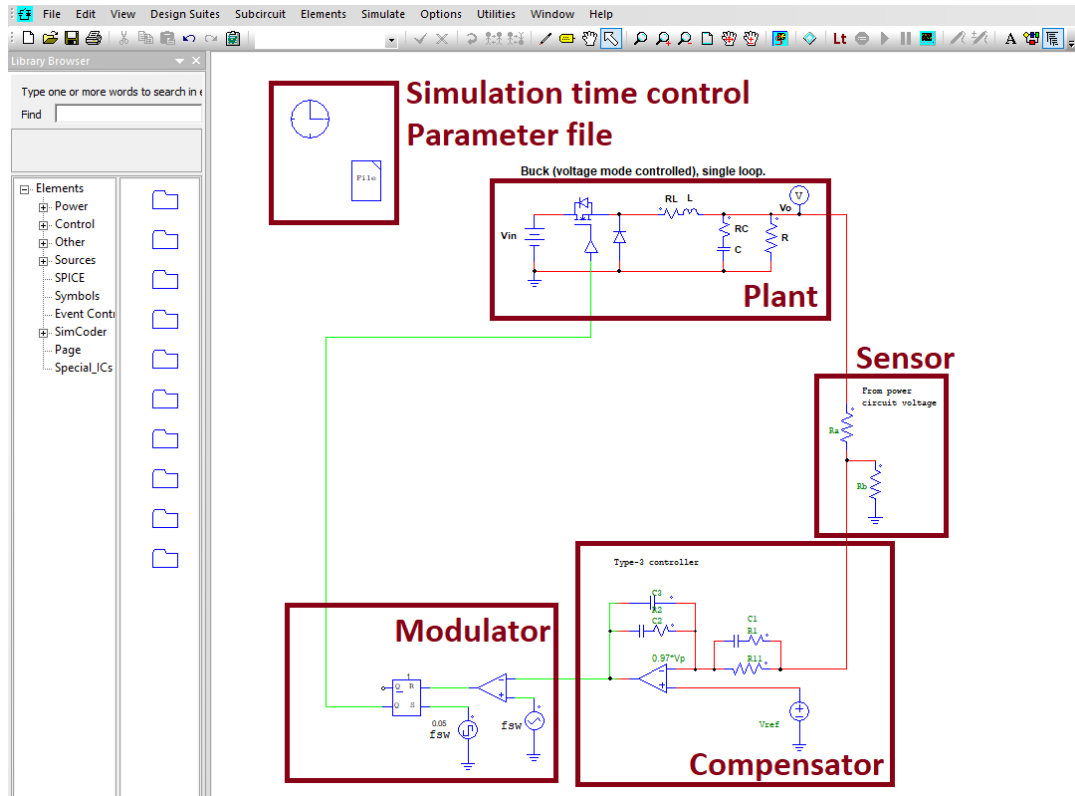


Figure 20: Psim exported system

In this picture, all the different functional blocks have been highlighted. Ensure to configure the simulation time control as follows. Figure 21.

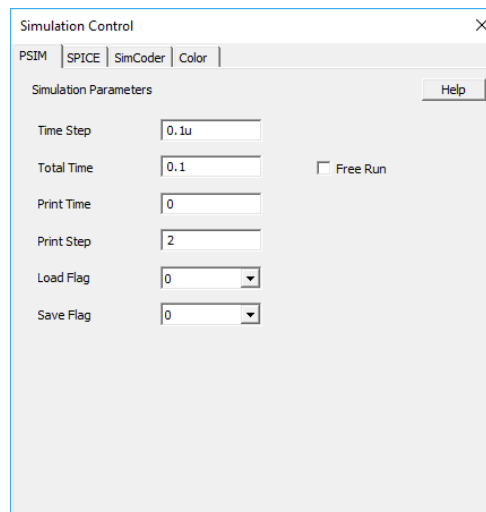


Figure 21: clock configuration in Psim

The result of the simulation is shown in Figure 22:

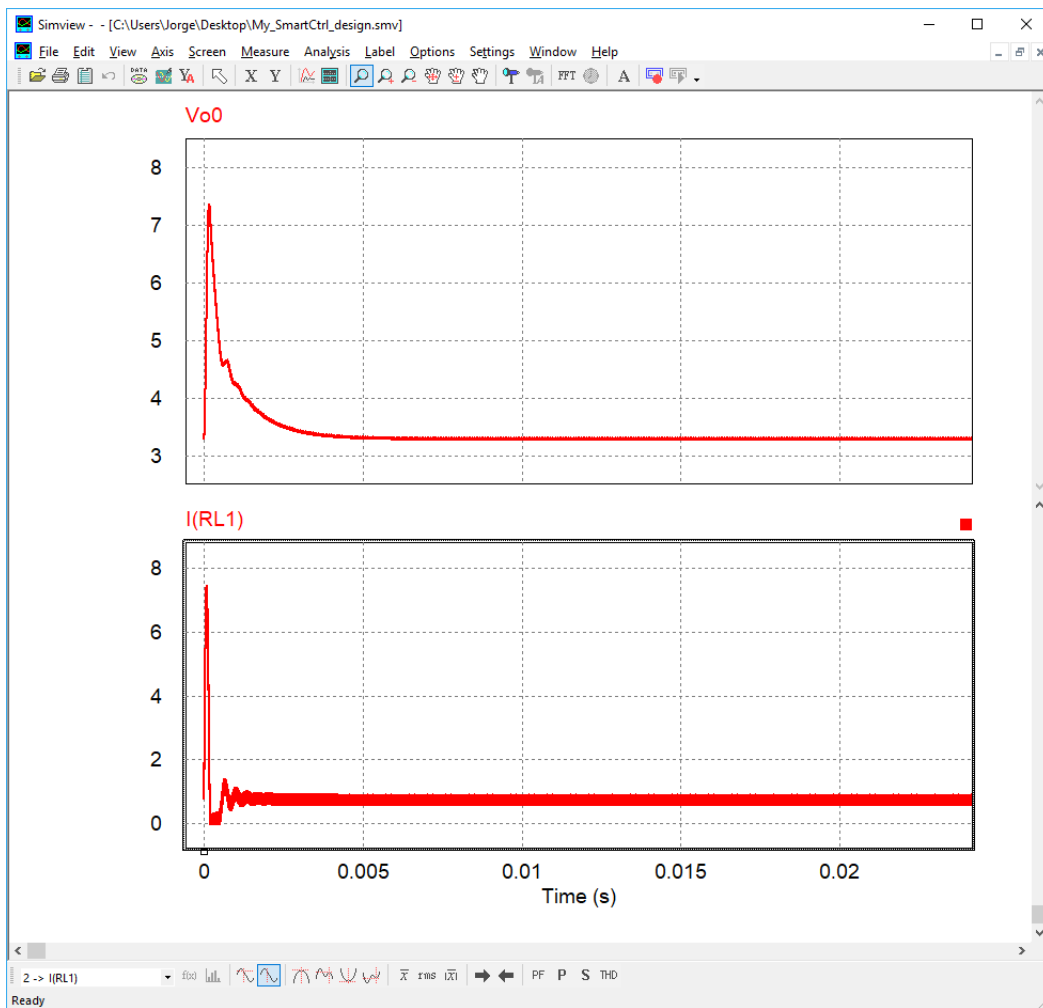


Figure 22: result of Psim simulation

As it can be seen, the output voltage is 3.3V, it is exactly what have been specified in SmartCtrl.

If the dynamic response of the system is to be analyzed, it would be necessary to introduce a step, for example, in the input voltage. See Figure 23.

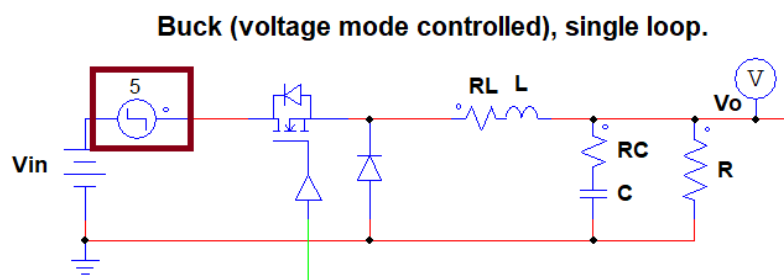


Figure 23: input voltage step in Psim

The result of this new system can be seen in Figure 24.

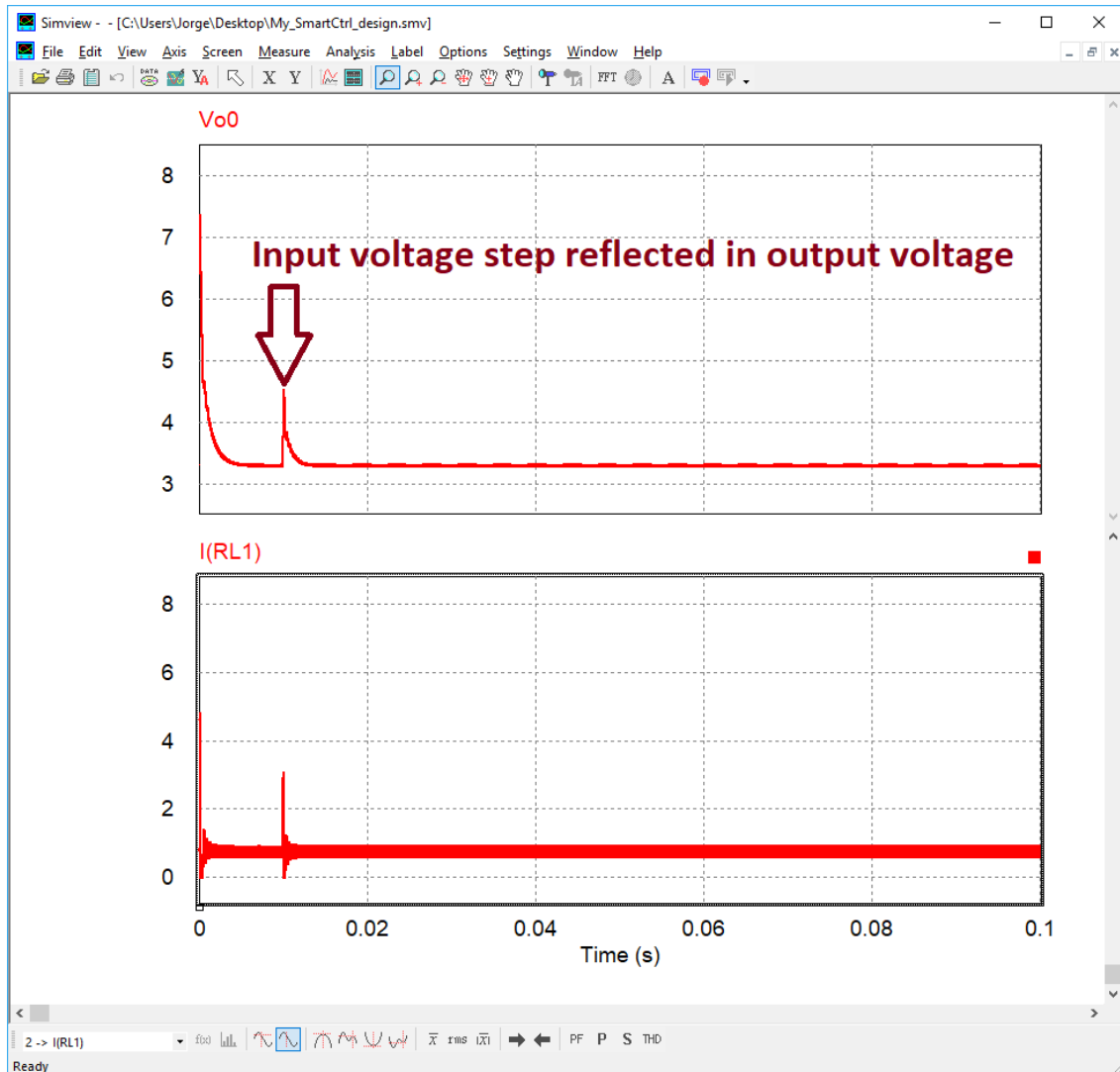


Figure 24: New Psim simulation where dynamic response can be seen